

### LAB 3 STRUCTURAL REPORT

Academic Integrity (more info @ <https://aisc.uci.edu/>): You are encouraged to discuss the labs at a high level, but the code/equations/simulations you come up with should be your own. By typing “yes” at the end of this question and filling in your name, you certify that the work you are turning in is your own work. Is the work you are turning in your own? yes

If you worked on any portion of your report or vhdl code with other students (discussion at high level & debugging; if more, please describe), please list their names here: \_\_\_\_\_

Student Name: Andy Tran

Student ID: 57422363

Date Completed: 5/16/2021

Time Spent: Reviewing Digital Design Material: 1 Hour

Design/Preparation Work: 2 Hours

VHDL Coding & Debugging: 3 Hours


### STRUCTURAL OVERVIEW

Replace this text w/ the % you feel you completed the lab. Be sure to list your general procedure of how you completed this lab & material (if any) you reviewed to help you complete this lab. Regardless of % stated, provide any details of difficulties (if any) you encountered during this lab. A few sentences are sufficient.

I think I did 100% of the lab, I filled in the Comblogic and StateRegister for the controller, then created signals and mapped them to the components so the signal went to the right places. I rewatched the Integrator Example and read through chapter 4 and 5 of the VHDL Design Book. Then created the fsm and chart and then implemented into code.
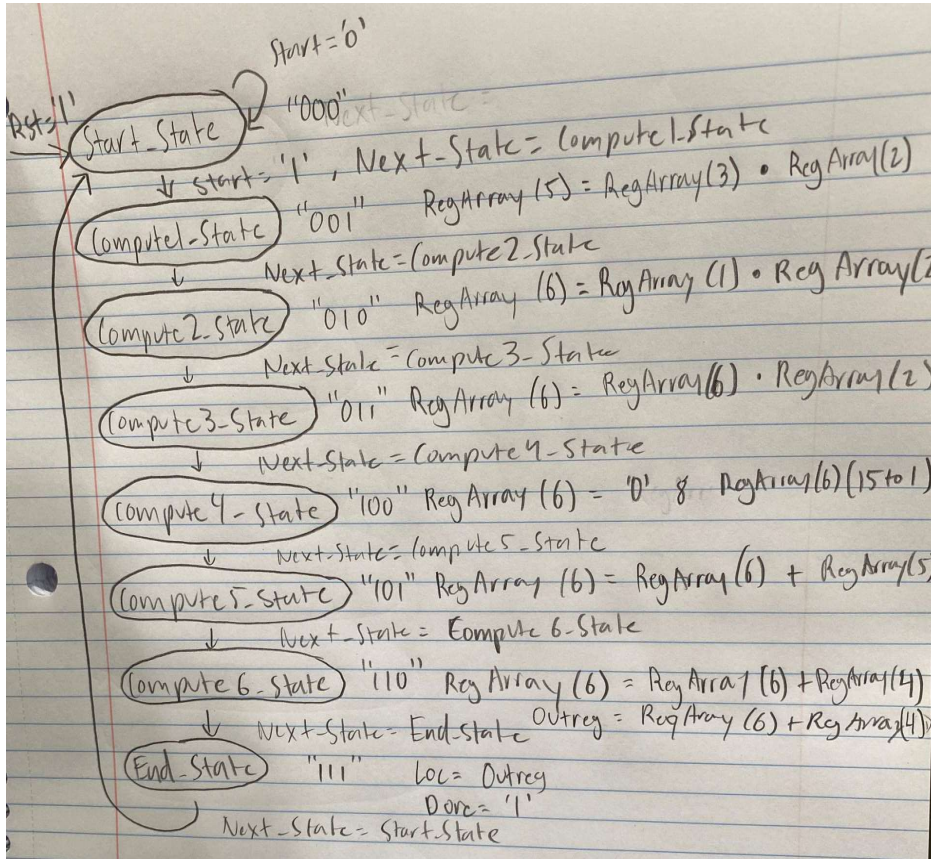
### LAB 3 FSMD & CONTROL WORD TABLE

Show your final FSMD here (even if nothing's changed). Explain why anything has changed or hasn't changed.



Show your control word table for your design here.

State-Ex	Start	Cur State	Next State	R.en	W.en	R.addr1	R.addr2	W.addr	Sh.sel	Sel.sel	ALU.sel	Oe	OutReg-ld	Done
S→C1	1	000001	X	0	X	X	X	X	X	X	X	0	X	0
C1→C2	X	001010	1	1	011010101	X	1	1	0	0	0	0	0	0
C2→C3	X	010011	1	1	001010110	X	1	1	0	0	0	0	0	0
C3→C4	X	011100	1	1	110010110	X	1	1	0	0	0	0	0	0
C4→C5	X	100101	1	1	xxxx110110	0	0	X	0	0	0	0	0	0
C5→C6	X	101110	1	1	110101110	X	1	0	0	0	0	0	0	0
C6→E	X	110111	1	1	110100110	X	1	0	0	1	0	0	0	0
E→S	X	111000	1	X	X	X	X	X	X	X	1	X	1	1

### LAB 3 MINIMUM CLOCK CYCLE

Minimum clock cycle: 37

Explain how you derived your minimum clock cycle (as discussed in class) here.

I derived the minimum clock cycle from watching the video and also reading the minimum clock delay in the book. It is the longest path from a clock to a clock, the register file does have one but when we are reading it is not necessary. So we start with 4 ns for the state register, then 11 ns for the comblogic, then 6 ns for the register file, then 12 ns for the ALU, then 3 ns for the selector, and finally 1 ns for setup time.

$$4 + 11 + 6 + 12 + 3 + 1 = 37 \text{ ns}$$

### LAB 3 STRUCTURAL SIMULATION GRAPH

Show a screenshot of your final graph here. You should crop it to the appropriate size so that it is legible.



### LAB 3 STRUCTURAL AND BEHAVIORAL SIMULATION GRAPH COMPARISONS

Compare your behavioral & structural graphs here. If there are any differences (delays, outputs, etc.), be sure to explain them here.

The differences between the graphs are that in the structural the output comes out much later because they are more states that compute the final location and also the clock cycle is much greater due to the delays of the components.