

LAB 1 BEHAVIORAL REPORT

Academic Integrity (more info @ <https://aisc.uci.edu/>): You are encouraged to discuss the labs at a high level, but the code/equations/simulations you come up with should be your own. By typing “yes” at the end of this question and filling in your name, you certify that the work you are turning in is your own work. Is the work you are turning in your own? **yes**

If you worked on any portion of your report or vhdl code with other students (discussion at high level & debugging; if more, please describe), please list their names here: _____

Student Name: **Andy Tran**

Student ID: 57422363

Date Completed: 4/8/21

Time Spent: Reviewing Digital Design Material: 2 hours

Design/Preparation Work: 1 hour

VHDL Coding & Debugging: 30 minutes

BEHAVIORAL OVERVIEW

What % do you feel you completed on the lab? Be sure to list your general procedure of how you completed this lab & material (if any) you reviewed to help you complete this lab.

Regardless of % stated, provide any details of difficulties (if any) you encountered during this lab. A few sentences are sufficient.

I feel like I have completed 100% of this lab. I watched the first lectures to see how to get started as this is our first lab. Then I read the prompt, then created a truth table, k map, boolean expression, and delay. Then I reread the drivelock exmaple to see how to build the process for the boolean expression to be put in. I did not really have difficulties.

LAB 1 TRUTH TABLE

Provide your truth table for Lab 1 here. You can create a table in Word, Excel, or attach a picture of your truth table as long as it is legible and in the correct orientation.

F3	F2	F1	F0	FWL
0	0	0	0	1
0	0	0	1	1
0	0	1	0	1
0	0	1	1	1
0	1	0	0	0
0	1	0	1	0
0	1	1	0	0
0	1	1	1	0
1	0	0	0	0
1	0	0	1	0
1	0	1	0	0
1	0	1	1	0
1	1	0	0	0
1	1	0	1	0
1	1	1	0	0
1	1	1	1	0

LAB 1 MINIMIZED EQUATION

Show the work you did to go from the truth table to your minimized equation here. Don't show your NAND/NOR/etc. conversions here, just the minimized Boolean equation that satisfies the requirements of the lab.

$F_3 F_2$ \ $F_1 F_0$	00	01	11	10
00	1	1	1	1
01	0	0	0	0
11	0	0	0	0
10	0	0	0	0

$FWL = F_3' F_2'$
 Delay is 3.4
 1 for inversion
 2.4 for AND

$$FWL = (F_3)' (F_2)'$$






LAB 1 ESTIMATED DELAY

List your estimated delay here (you are not required to add the delay to the actual vhdl code for behavioral): 3.4 ns

LAB 1 BEHAVIORAL SIMULATION GRAPH

Show a screenshot of your final graph here. You should crop it to the appropriate size so that it is legible.

Apologies for not being able to get the final graph into less screenshots, the black backgrounds makes the lines blend with less pixel. Every 10ns is the next step.

Name
 Fuel3
 Fuel2
 Fuel1
 Fuel0
 FuelWarningLight

